










## Year 7 Electricity fact sheet

Circuits and components		
1.		Switch (open)
2.		Cell
3.		Battery
4.		Lamp / bulb
5.		Voltmeter
6.		Ammeter
7.		Resistor
Series circuits		
8. What type of circuit is shown below?		Series
9. What happens to the brightness of the lamps when you add more lamps in the series circuit?	They get less bright/ they get dimmer	

## Year 7 Electricity fact sheet

<b>Parallel circuits</b>	
<p><b>10. What type of circuit is shown below?</b></p> 	<p><b>Parallel</b></p>
<p><b>11. How is a parallel circuit different to a series circuit?</b></p>	<p><b>A parallel circuit has branches in it</b></p>
<p><b>12. What happens to the brightness of the lamps when you add more lamps into a parallel circuit?</b></p>	<p><b>They stay the same brightness</b></p>
<b>Current in circuits</b>	
<p><b>13. What do we call the flow of electrical charge in a wire?</b></p>	<p><b>Current</b></p>
<p><b>14. State the units for current</b></p>	<p><b>A (amps)</b></p>
<p><b>15. What do we use to measure current?</b></p>	<p><b>Ammeter</b></p>
<p><b>16. Which number shows the correct place to put an ammeter into the circuit?</b></p>	
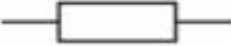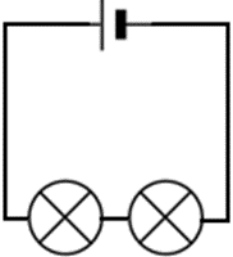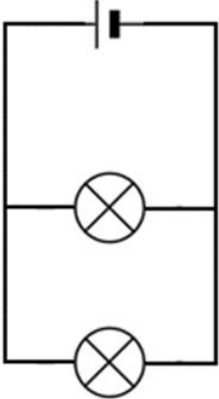
## Year 7 Electricity fact sheet

17. In a series circuit, the current is _____ through each component	the same
18. In a parallel circuit, the current is _____ between the components	shared
<b>Voltage in circuits</b>	
<b>19. State the units for voltage</b>	V (volts)
<b>20. What do we use to measure voltage?</b>	Voltmeter
21. Which number shows the correct place to put a voltmeter into the circuit?	
22. In a series circuit, the voltage is _____ between the components	shared
23. In a parallel circuit, the voltage is _____ across each component	the same

## Year 7 Electricity fact sheet

Resistors	
24. What does a resistor do to the current in a circuit?	Makes it less/ reduces it
25. How do you calculate resistance, when you know the voltage and current?	Resistance = voltage $\div$ current
26. State the units for resistance	$\Omega$ (ohms)
27. In a circuit, the voltage is 12V and the current is 3A. Calculate the resistance.	Resistance = voltage $\div$ current $= 12 \div 3$ $= 4 \Omega$
28. In a circuit, the voltage is 63V and the current is 9A. Calculate the resistance.	Resistance = voltage $\div$ current $= 63 \div 9$ $= 7 \Omega$